

Signal generators

Source of these slides

The following texts have also been used to prepare this lecture:

- A. S. Sedra, and K. C. Smith, Microelectronic Circuits. Oxford, 2011
- R.C. Jaeger, T.N. Blalock, Microelettronica. McGraw-Hill
- Thomas L. Floyd, Electronic Devices. --: Pearson Prentice Hall, 2005
- P. Horowitz and W. Hill, The art of electronics. --: Cambridge University Press, 2015
- Neil Storey, Electronics, A system approach. --: Pearson Prentice Hall, 2006
- V. K. Mehta, Principles of Electronics

Goal: to learn the operating principles of various circuits for signal generation based on op-amps and BJTs

Motivation: It is often necessary to design circuits for generating signals (square waves, triangular waves, sine waves).

Here we will analyze some examples. We will describe some basic circuits (based on op-amps and BJTs) for signal generation

Lab experiment → Wavefunction generator based on op-amps and BJTs

Motivation

In the design of electronic systems, signals having prescribed standard waveforms are frequently needed (sine, rectangular, triangular, pulse, ...)

Such signals are required

- **In computer and control systems** as clocks (for timing)
- **In communication systems**, to carry information
- **In test and measurement systems**, for testing and characterizing electronic devices and circuits


There are different approaches to generate sinusoids:

- **The use of positive-feedback loops**, consisting of an amplifier and a RC or LC network, based on the resonance phenomenon. These are often called **linear oscillators**.
- The use of **circuits that generate sinusoids by shaping triangular waves (non-linear oscillators)** → Circuits that generate square, triangular, pulse waveforms employing circuit blocks known as multivibrators (bistable, astable, monostable)

Here we will discuss some basic circuits based on the latter approach

The bistable circuit

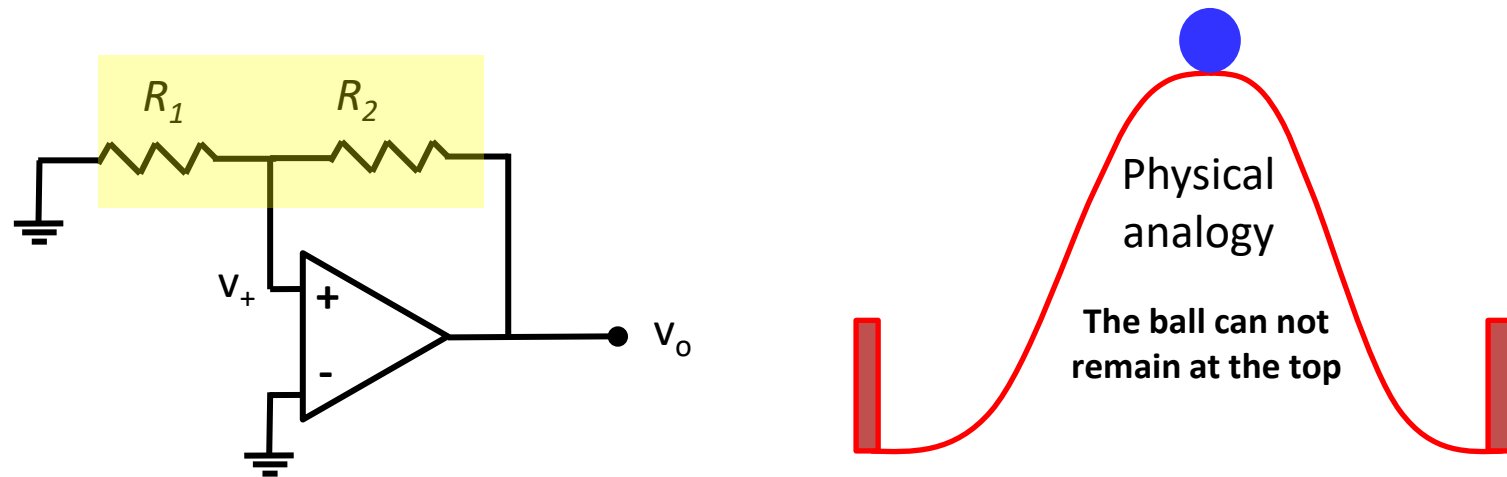
The bistable circuit has two stable states. The circuit can remain in either stable state indefinitely, and moves to the other state only when appropriately triggered



- Consider that the positive terminal v_+ is close to zero. Imagine that the electrical noise causes a small positive increment of voltage v_+ . This small signal will be amplified by the (large) gain of the op-amp, and a much greater signal will appear on the output v_o
- The voltage divider (R_1 , R_2) will feed a fraction $\beta = R_1 / (R_1 + R_2)$ of the output signal on v_+
- This process will continue until the op-amp reaches saturation at the positive maximum output (L_+)
- When this happens, the voltage at the positive input terminal v_+ becomes $L_+ R_1 / (R_1 + R_2)$
→ The output stays in this state **for ever!** → this is one of the stable states of the bistable


The bistable circuit

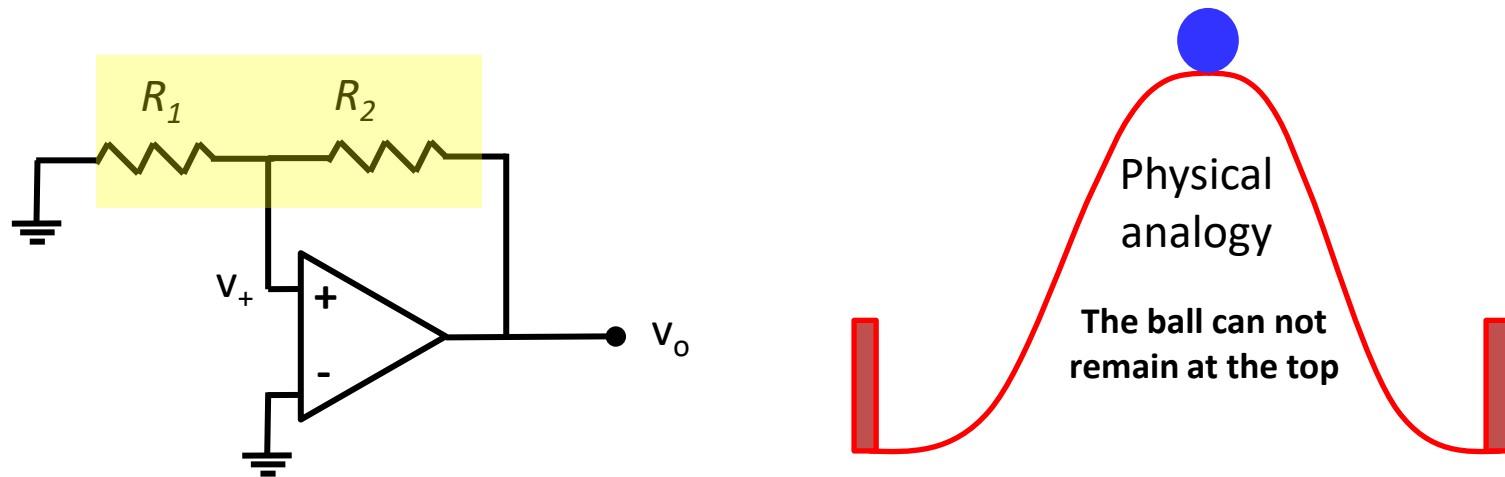The bistable circuit has two stable states. The circuit can remain in either stable state indefinitely, and moves to the other state only when appropriately triggered



- The same happens in the equally-probable case that v_+ starts from a slightly negative value \rightarrow In this case, the output voltage saturates to $v_o=L_-$
- The bistable circuit can remain in the saturated states indefinitely
- The circuit can not remain in the state where $v_+=0\text{ V}$ and $v_o=0\text{ V}$ \rightarrow Unstable equilibrium (metastable state). Any disturbance leads to a transition (contrary to the case where the feedback is negative, where the virtual short circuit reduces disturbances)

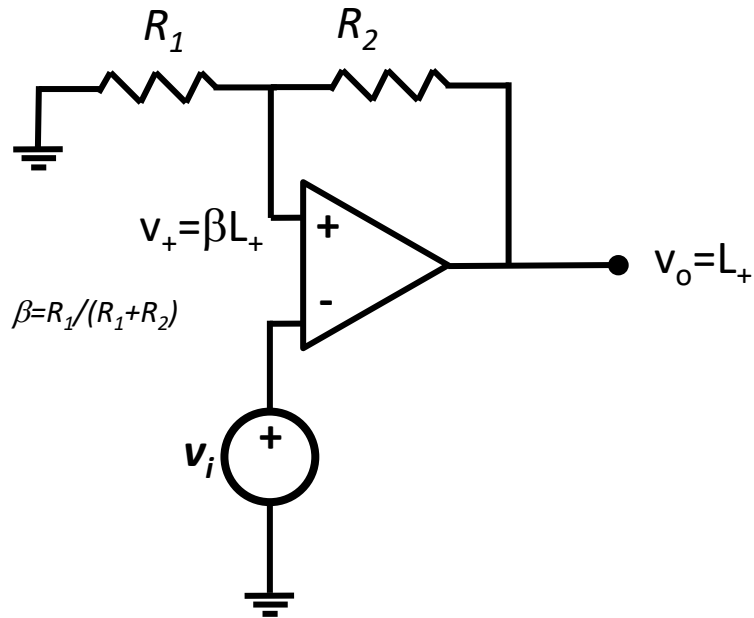Transfer characteristics of the inverting bistable circuit




To derive the transfer characteristic we assume that v_o is at L_+ , and thus $v_+ = \beta L_+$

As v_i is increased from 0 V, nothing happens until v_i reaches a value equal to $v_+ = \beta L_+ = V_{TH}$


As v_i exceeds this value, a net negative voltage appears at the input terminals of the op-amp, and v_o goes negative

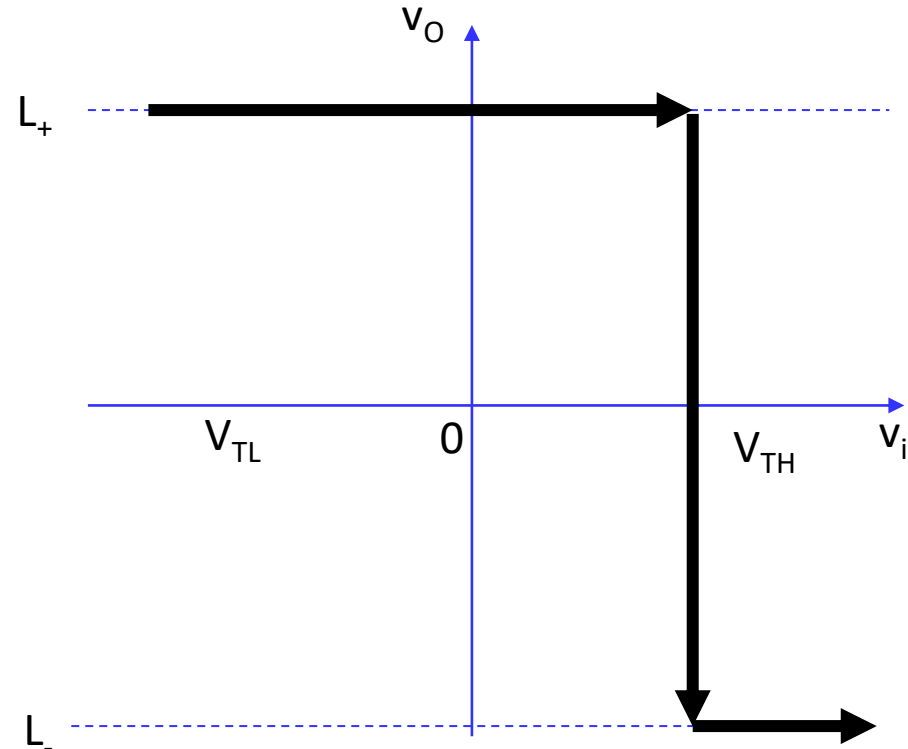How can we make this circuit change state?



The voltage divider causes v_+ to go negative, thus increasing the net negative input of the op-amp, and the output saturates to $v_o = L_-$

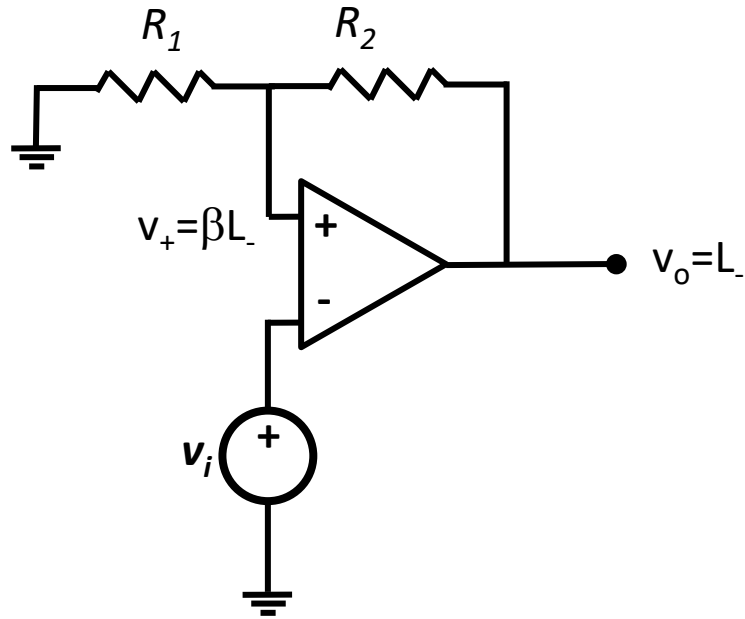Transfer characteristics of the inverting bistable circuit




When v_i is decreased \rightarrow since $v_+ = \beta L_-$, the output remains in negative saturation until v_i goes below $V_{TL} = \beta L_-$.

At this point, the output switches back to L_+ .


The circuit is said to exhibit hysteresis; the width of the hysteresis is the difference between the two thresholds, V_{TH} and V_{TL} .

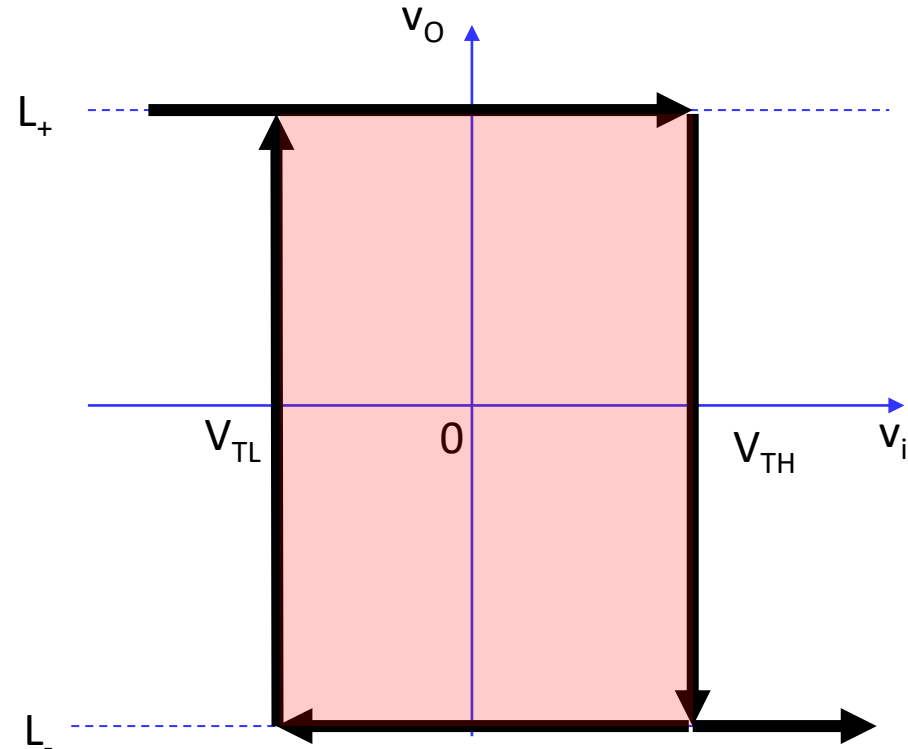How can we make this circuit change state?




This circuit is said to be inverting \rightarrow output goes negative with positive input!

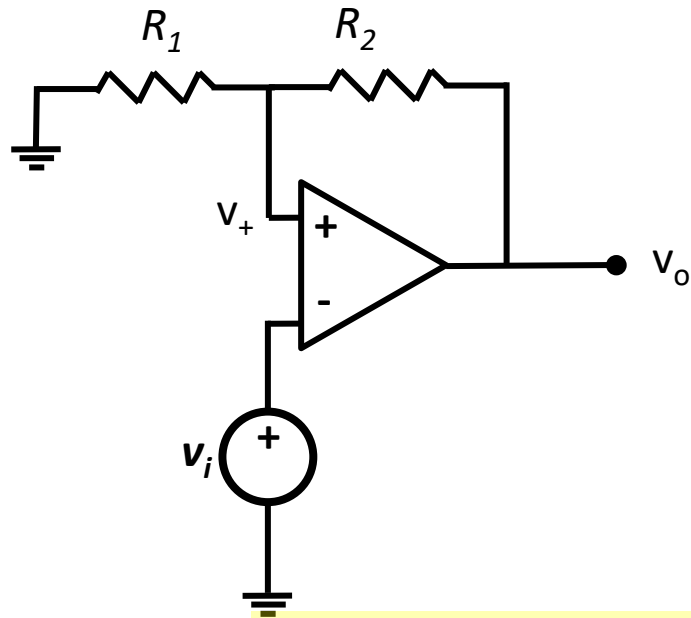Transfer characteristics of the inverting bistable circuit



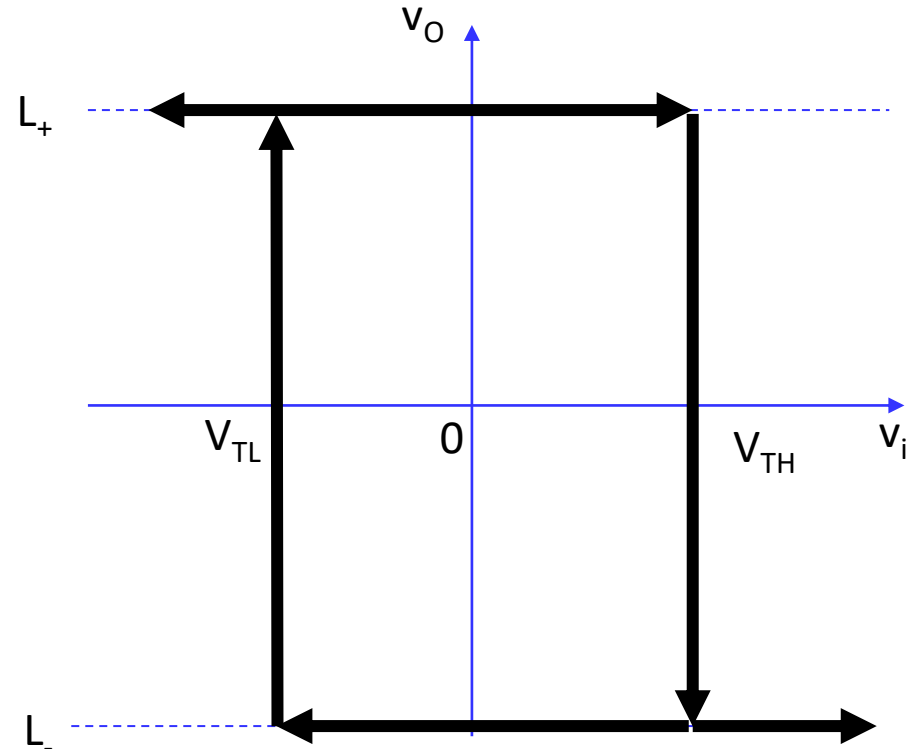How can we make this circuit change state?




We note that to change state it is not necessary to keep the v_i signal high or low → A pulse (trigger signal) is sufficient, then the system holds the new state until the input goes beyond the other threshold

The value of the output only depends on the previous value of the trigger signal (the trigger that caused the circuit to be in its current state) → thus the circuit exhibits **memory** (this is a basic memory element of digital systems)

In analog circuit applications, the bistable circuit is also known as Schmitt trigger

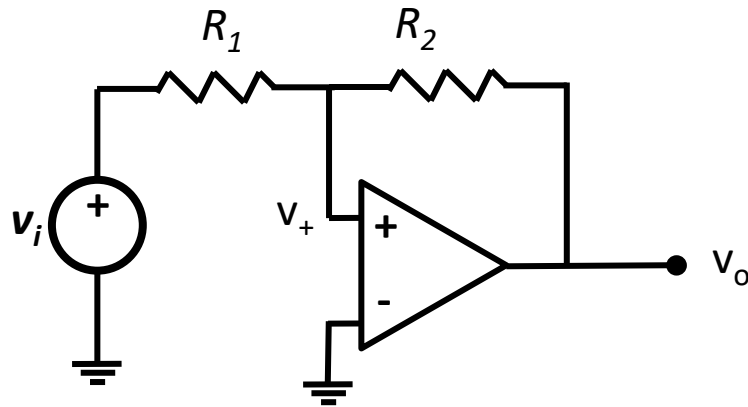
Bistable circuit with non-inverting transfer characteristic



The basic bistable feedback loop can be used to derive a circuit with noninverting transfer characteristics, by applying the input signal v_i to the terminal of R_1

To obtain the transfer characteristic we use the superposition

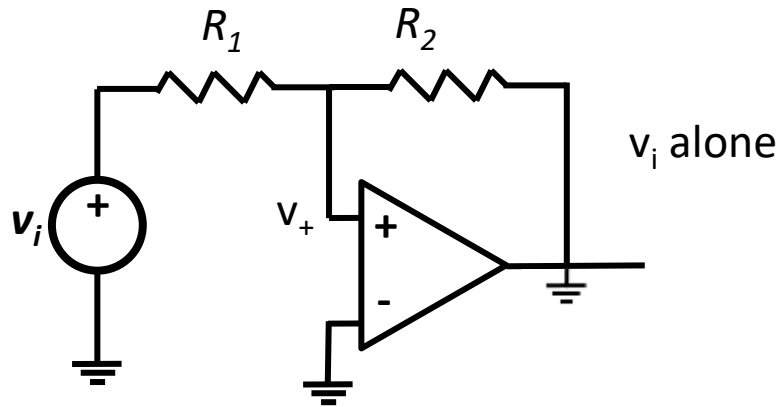
Bistable circuit with non-inverting transfer characteristic



The basic bistable feedback loop can be used to derive a circuit with noninverting transfer characteristics, by applying the input signal v_i to the terminal of R_1

To obtain the transfer characteristic we use the superposition

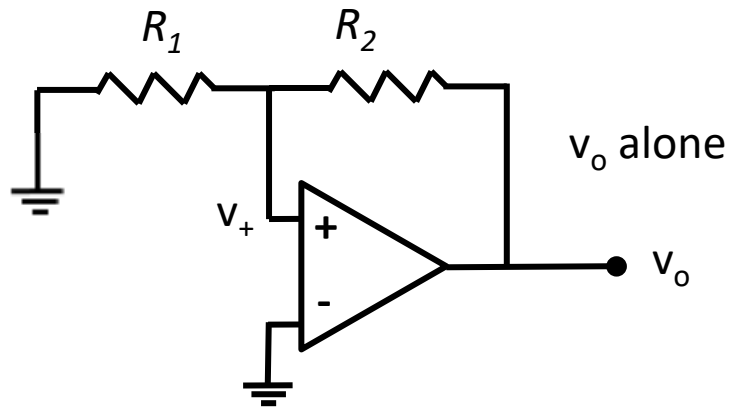
Bistable circuit with non-inverting transfer characteristic



The basic bistable feedback loop can be used to derive a circuit with noninverting transfer characteristics, by applying the input signal v_i to the terminal of R_1

To obtain the transfer characteristic we use the superposition

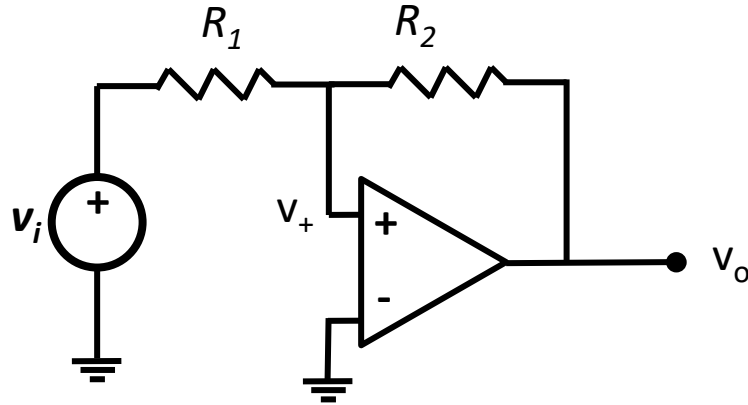Bistable circuit with non-inverting transfer characteristic



If $v_o = L_+$, positive values of v_i will have no effect. To trigger the circuit into the L_- state, v_i must be made negative


V_{TL} can be found by substituting $v_o = L_+$, $v_+ = 0$, $v_i = V_{TL}$

And the result is $V_{TL} = -L_+ (R_1 / R_2)$


The basic bistable feedback loop can be used to derive a circuit with noninverting transfer characteristics, by applying the input signal v_i to the terminal of R_1

To obtain the transfer characteristic we use the superposition:
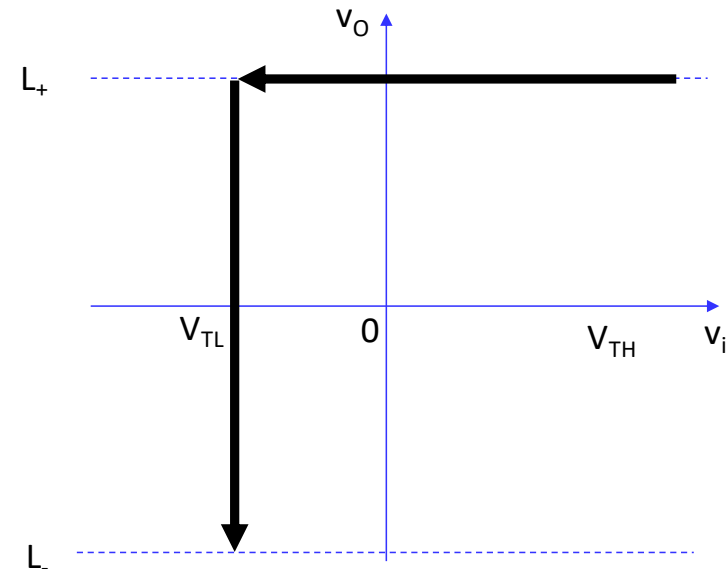
$$v_+ = v_i \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2}$$



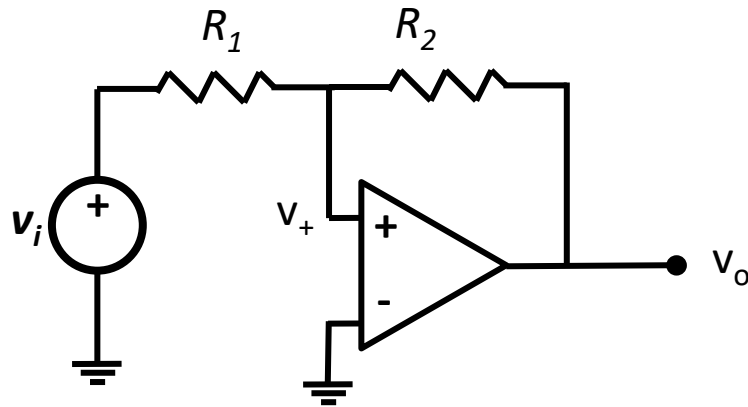Bistable circuit with noninverting transfer characteristic



Similarly, if $v_o = L_-$, negative values of v_i will have no effect. To trigger the circuit into the L_+ state, v_i must be made positive


V_{TH} can be found by substituting $v_o = L_-$, $v_+ = 0$, $v_i = V_{TH}$

And the result is $V_{TH} = -L_- (R_1 / R_2)$


The basic bistable feedback loop can be used to derive a circuit with noninverting transfer characteristics, by applying the input signal v_i to the terminal of R_1

To obtain the transfer characteristic we use the superposition:
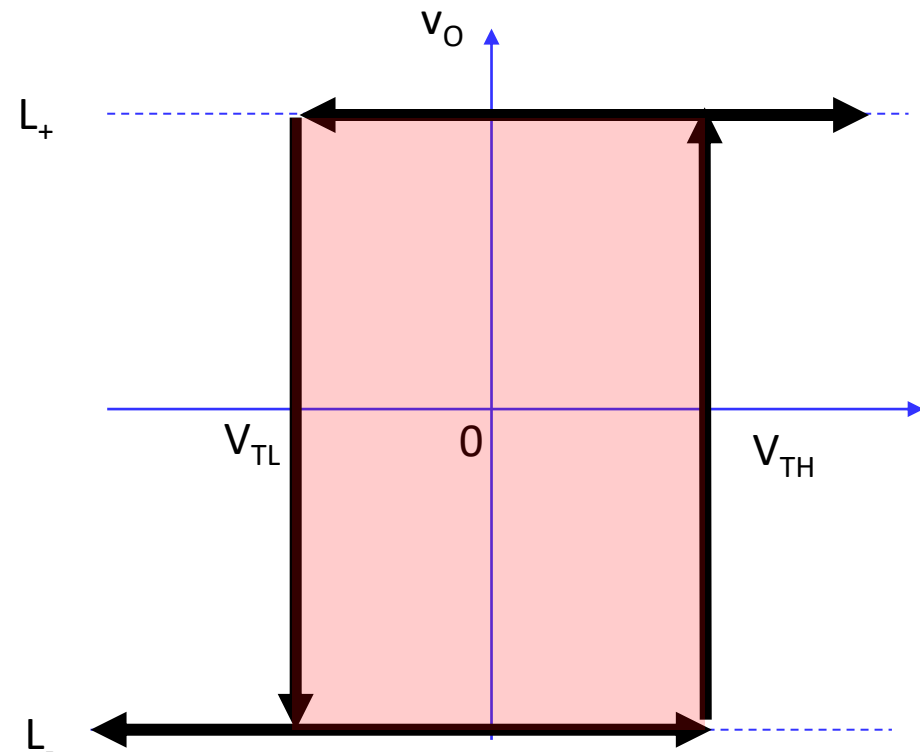
$$v_+ = v_i \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2}$$





Bistable circuit as comparator

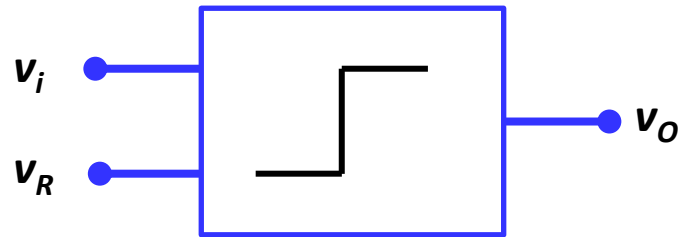


The comparator is an analog circuit building block that is used for several applications:

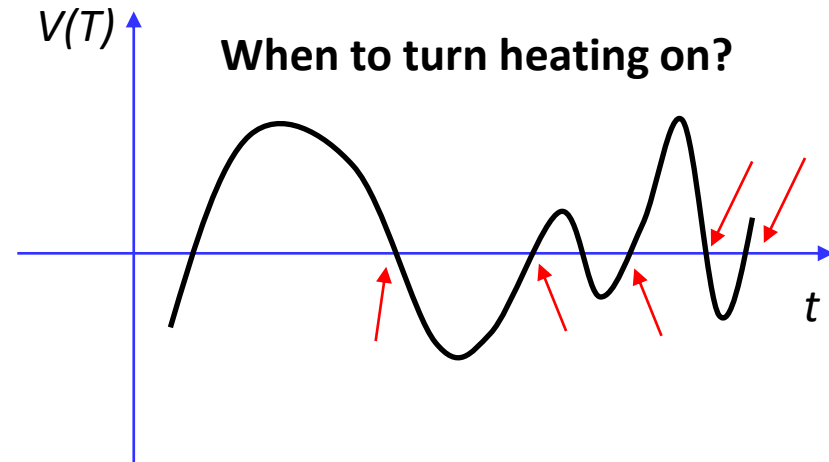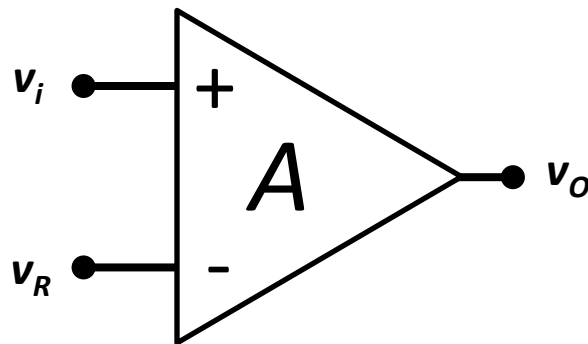- Detecting the level of a signal with respect to a threshold
- Design of A/D converters
- ...



Bistable circuit as comparator


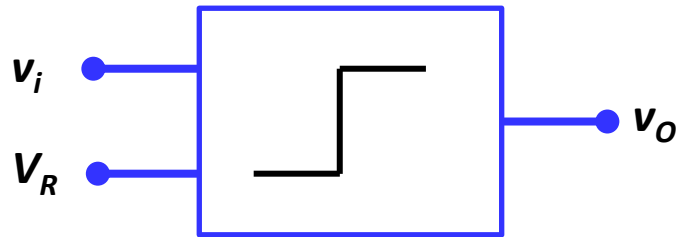


The comparator is an analog circuit building block that is used for several applications:

- Detecting the level of a signal with respect to a threshold
- Design of A/D converters
- ...


In several applications a single threshold is not sufficient, and hysteresis (i.e. two thresholds) can help!

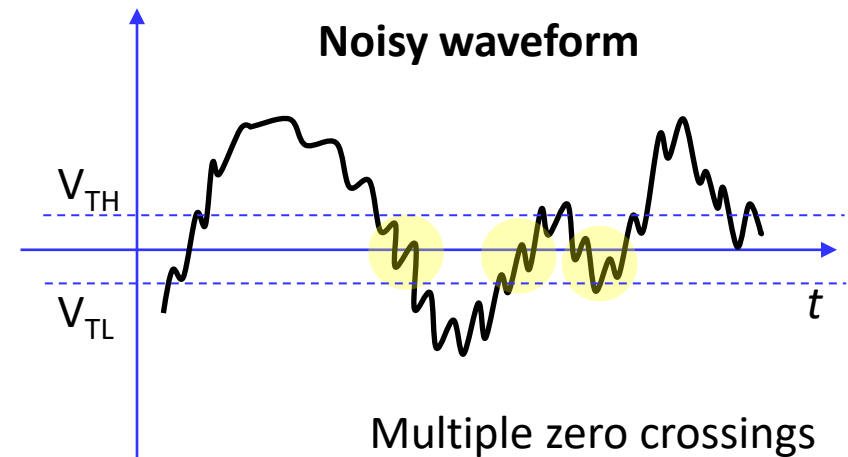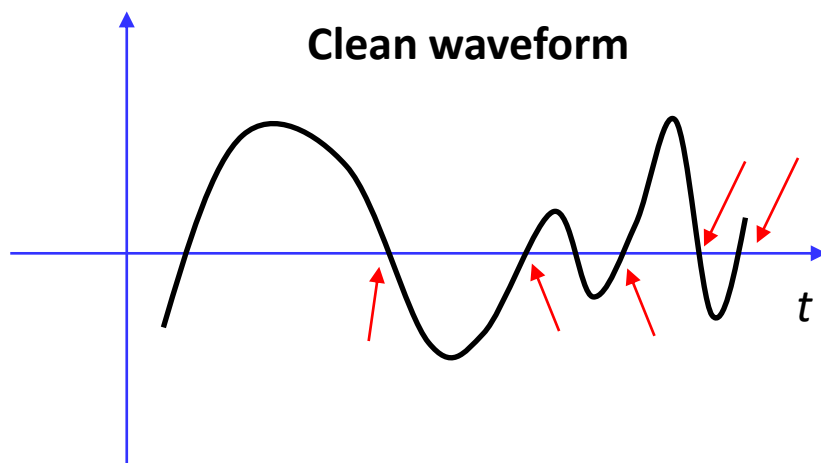An example is the circuit for detecting the zero crossing of an arbitrary waveform



Multiple zero crossings

Bistable circuit with offset (inverting)

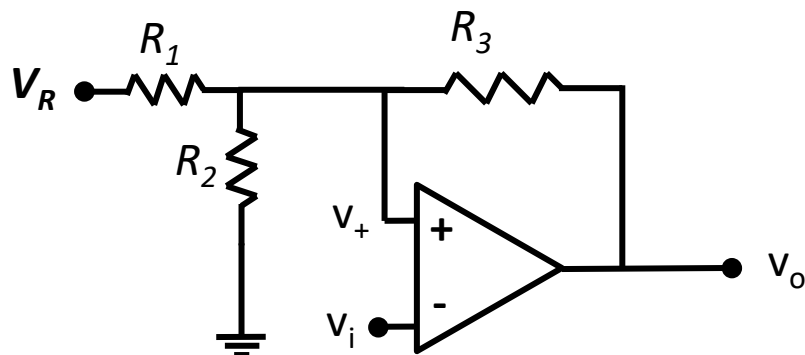

To obtain the transfer characteristic we use the superposition:


$$v_+ = V_R \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + v_o \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$

When $v_o = L_+$

$$V_{TH} = V_R \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + L_+ \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$

When $v_o = L_-$
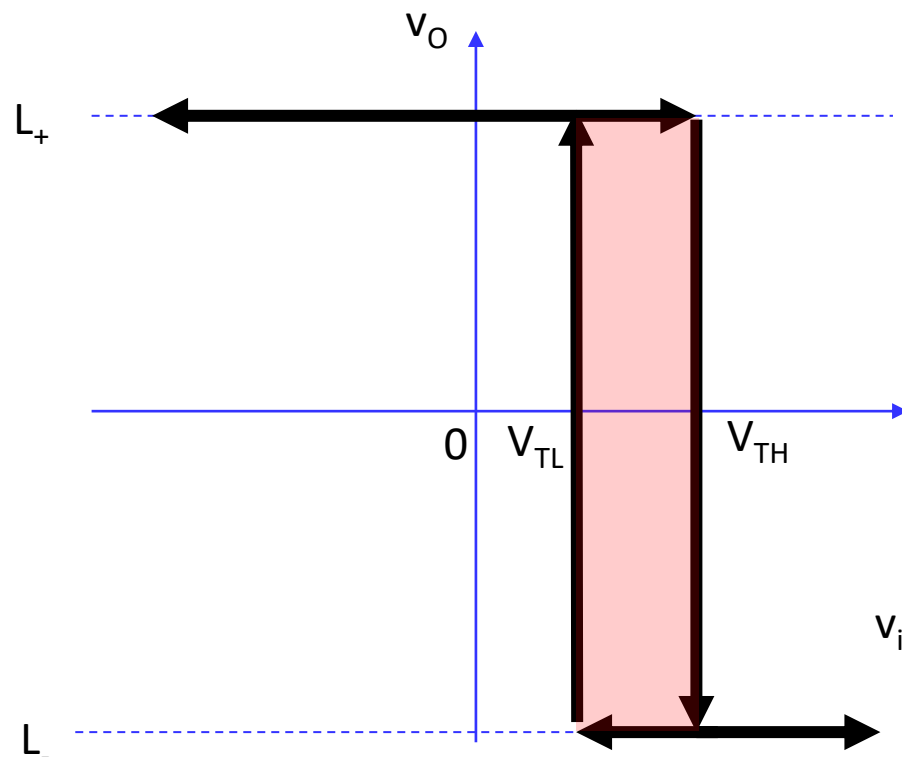
$$V_{TL} = V_R \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + L_- \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$



Numerical example:


If $R_1=10 \text{ k}\Omega$, $R_2=10 \text{ k}\Omega$, $R_3=100 \text{ k}\Omega$, $V_R=5 \text{ V}$, $L_+=L_-=5 \text{ V}$, the two thresholds are:

$$V_{TH}=2.62 \text{ V}$$

$$V_{TL}=2.14 \text{ V}$$

How to make the output voltage more accurate?

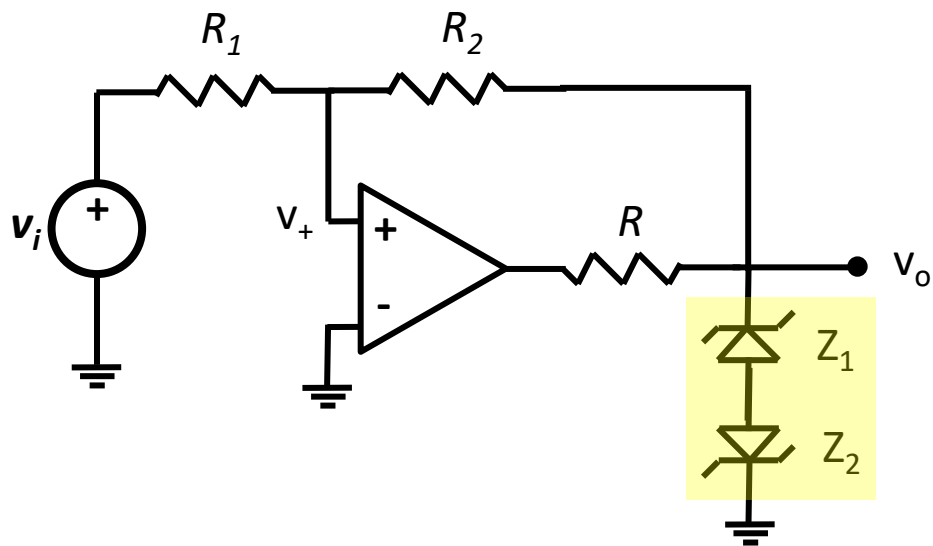We know that the saturation voltage of the op-amp is never equal to $V_{CC}/-V_{EE}$... how to make the output more precise? → **By cascading the op-amp with a limiter circuit!**



In this circuit, the value of R should be chosen to yield the current required for the proper operation of the zener diodes ($I_z > I_{zmin}$)


For this circuit:

- $L_+ = V_{Z1} + V_D$
- $L_- = -(V_{Z2} + V_D)$

Where V_D is the drop on a forward-biased diode

How to make the output voltage more accurate?

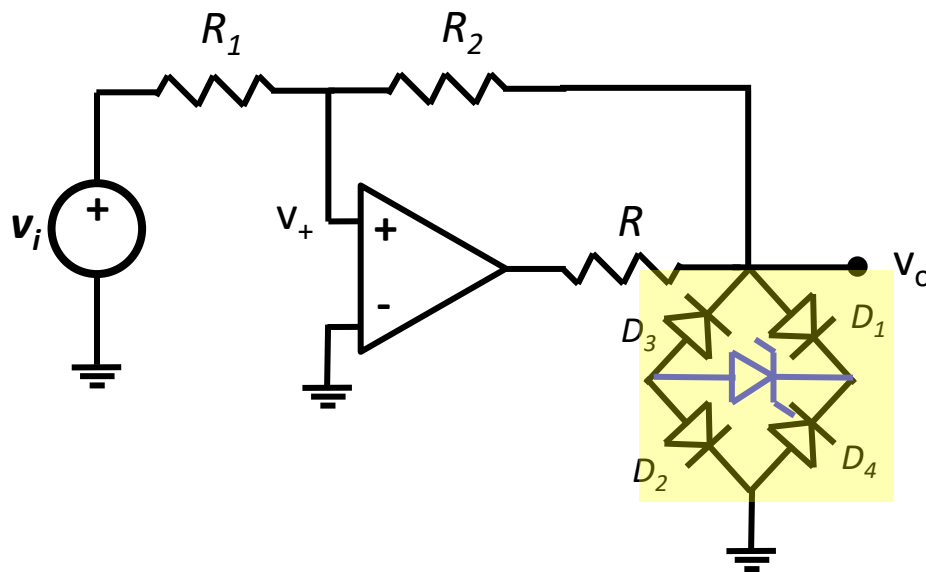We know that the saturation voltage of the op-amp is never equal to $V_{CC}/-V_{EE}$... how to make the output more precise? → **By cascading the op-amp with a limiter circuit!**






In this circuit, the value of R should be chosen to yield the current required for the proper operation of the zener diodes




For this circuit:

- $L_+ = V_Z + V_{D1} + V_{D2}$
- $L_- = -(V_Z + V_{D3} + V_{D4})$

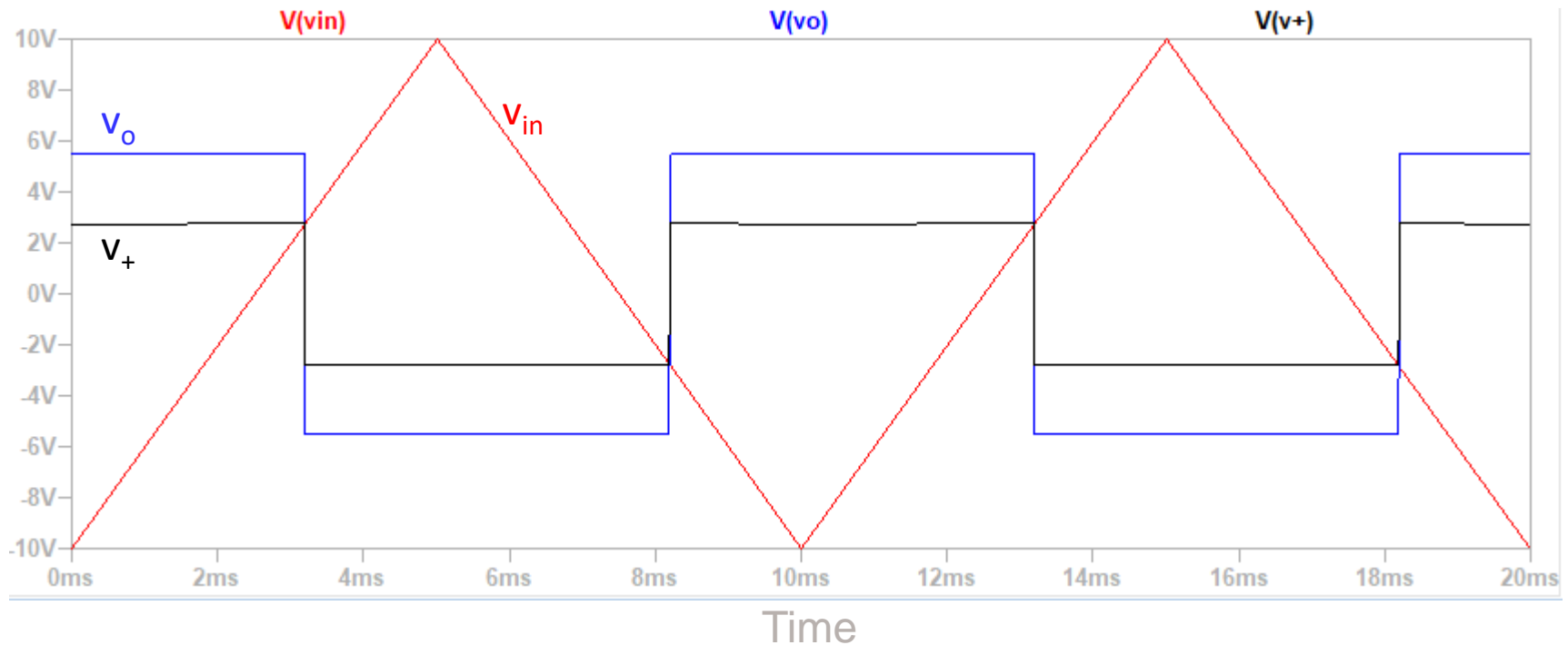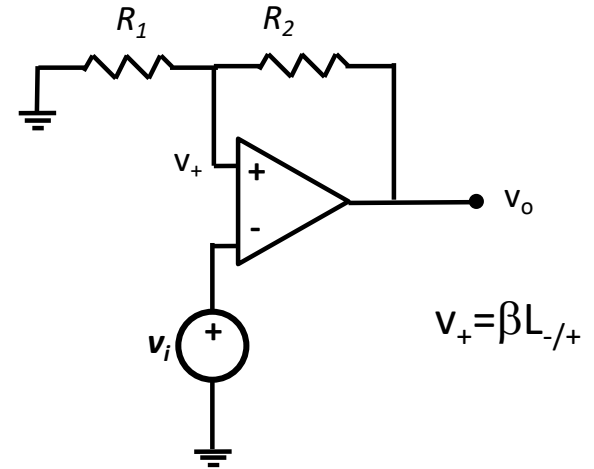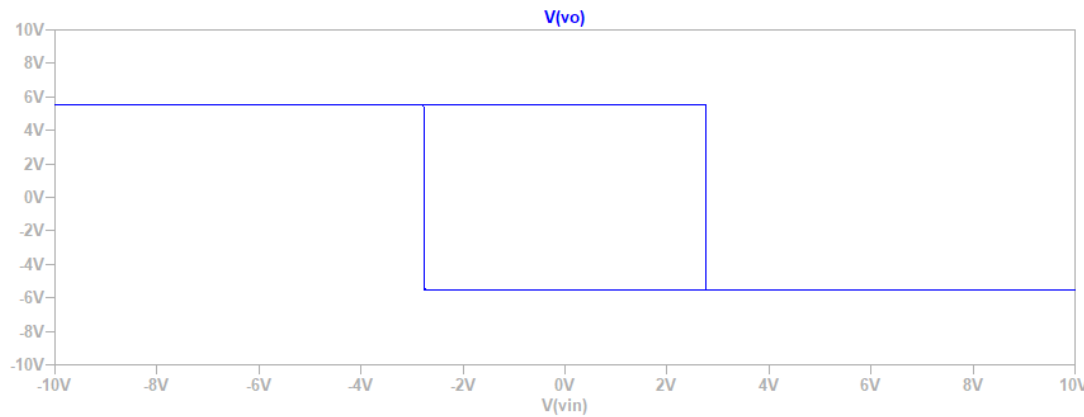
How to measure the transfer characteristics with LTspice?



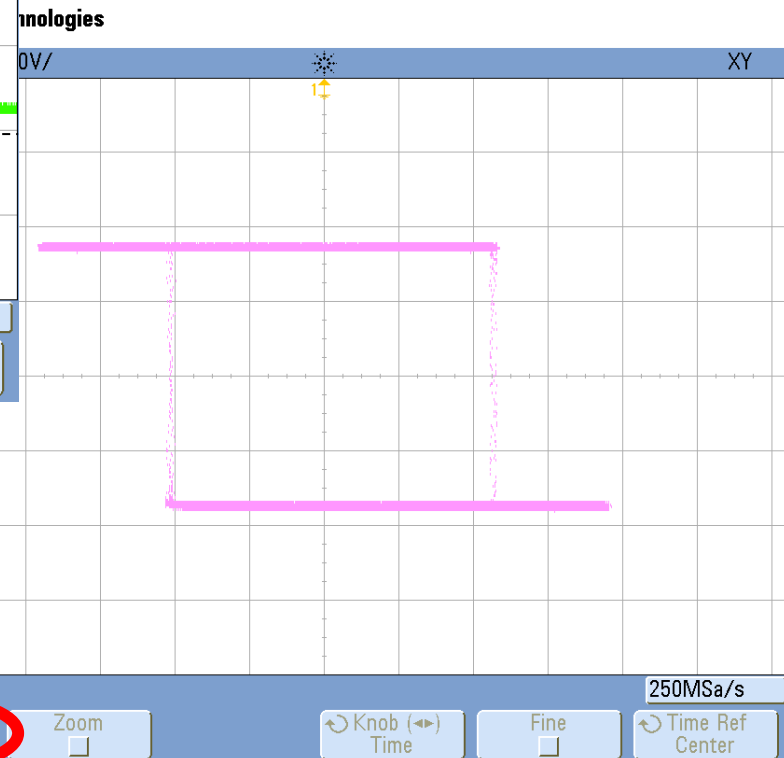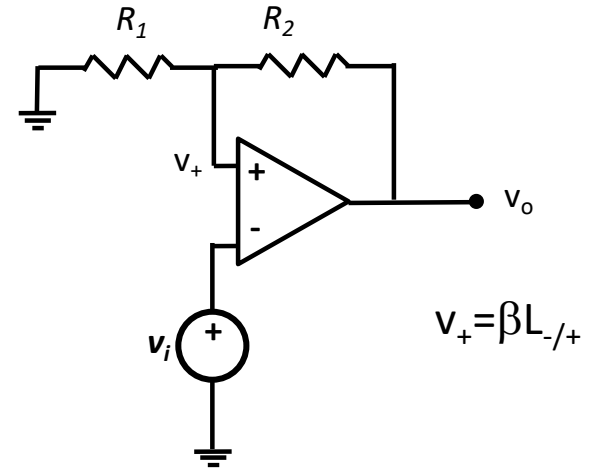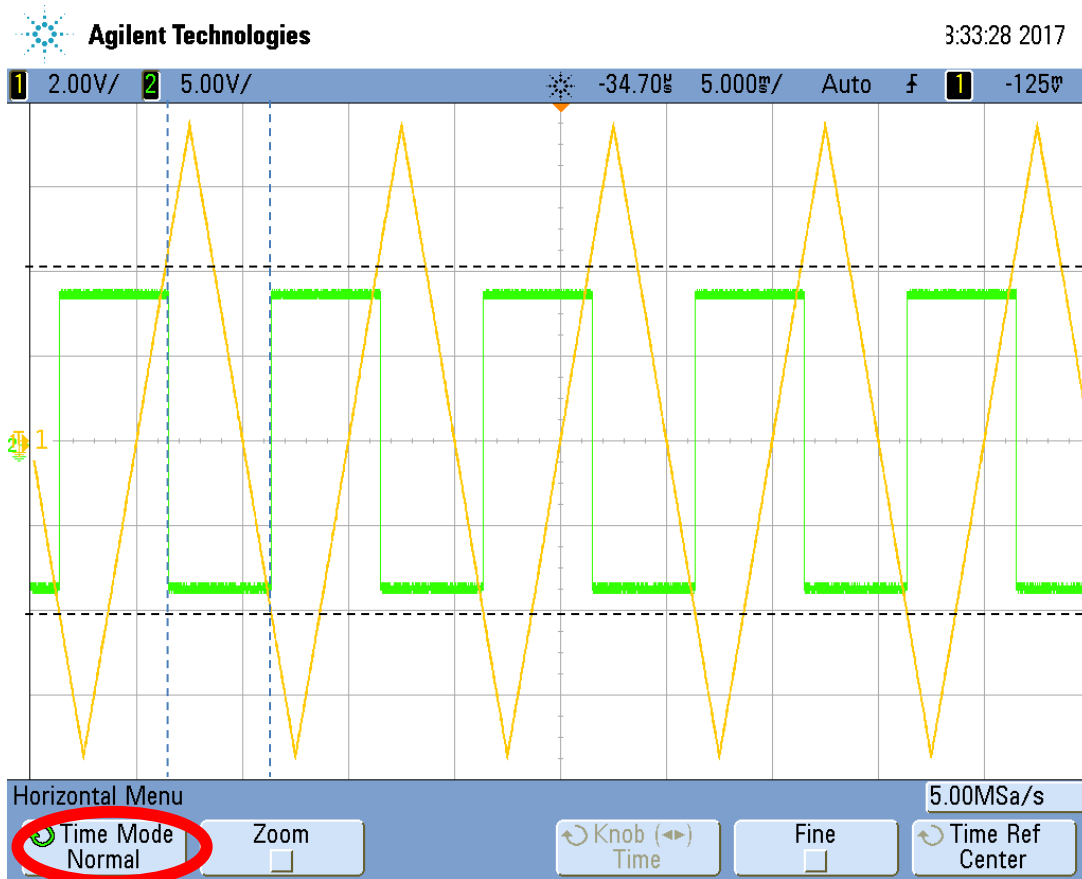How to measure the transfer characteristics with a scope?



Generation of triangular waveforms


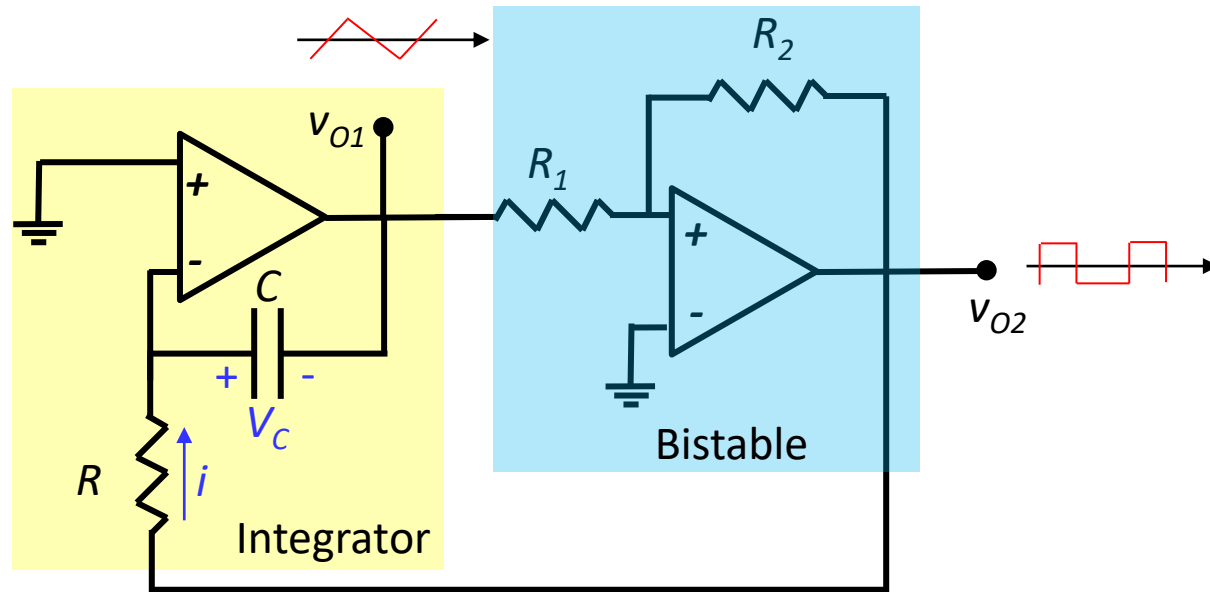


Square waves can be generated by forcing a bistable circuit to change state continuously

In this case, an integrator is connected to the output of the bistable circuit to form a triangular wave

The circuit has two outputs: triangular wave and square wave. The timing (period) of the two waves is defined by the properties of the RC network

Generation of triangular waveforms

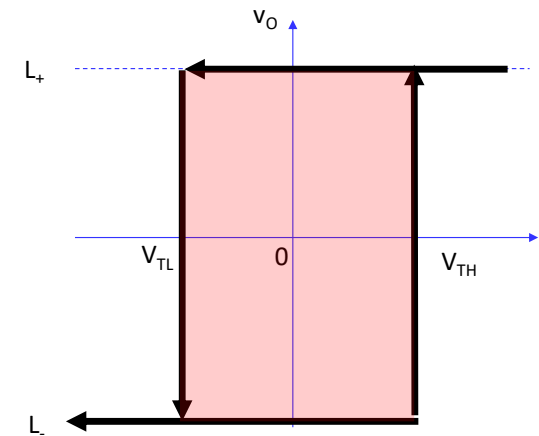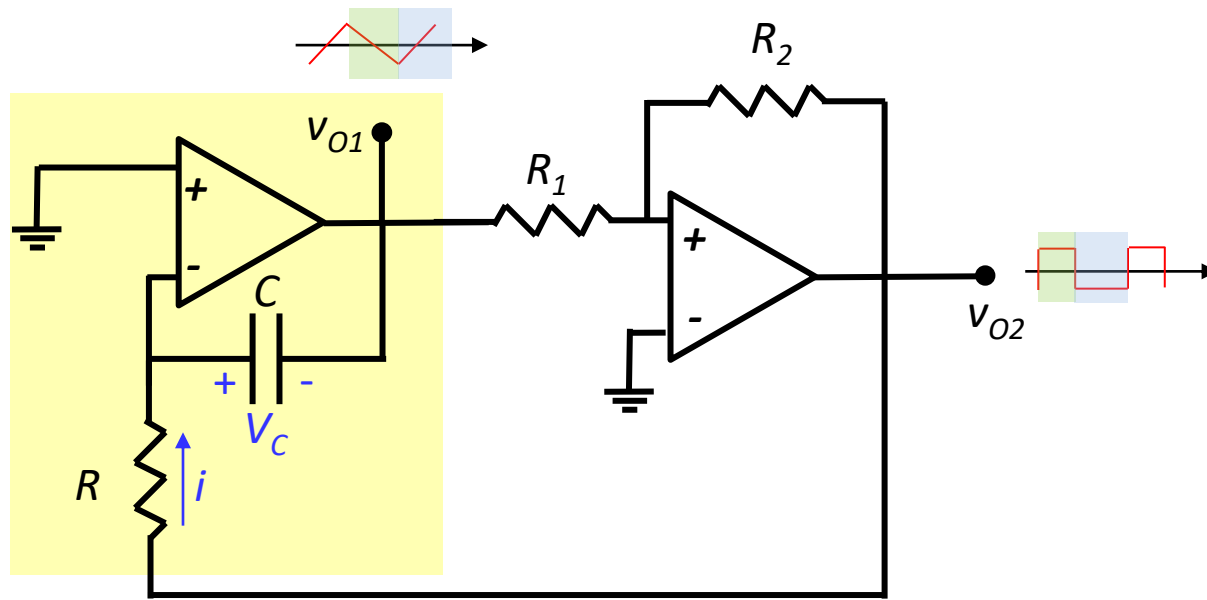


Consider the output v_{O2} to be at L_+ . The current on R is equal to $i = L_+/R$, and is **constant**

This will cause the output of the integrator **to linearly decrease** with a slope of $-L_+/RC$

$$i = C \frac{dV_C}{dt} = -C \frac{dV_{O1}}{dt} = \frac{L_+}{R} \longrightarrow \frac{dV_{O1}}{dt} = -\frac{L_+}{RC} \longrightarrow V_{O1}(t) = V_{O1}(0) - \int \frac{L_+}{RC} dt = V_{O1}(0) - \frac{L_+ t}{RC}$$


This process continues until v_{O1} reaches the lower threshold of the bistable circuit, V_{TL} at which point the bistable circuit will switch state, its output v_{O2} becoming equal to L_- . The current on the capacitor will reverse direction, its absolute value becoming equal to $|L_-|/R$. The integrator output will start to increase linearly with slope equal to $|L_-|/RC$ until V_{TH} is reached

Generation of triangular waveforms

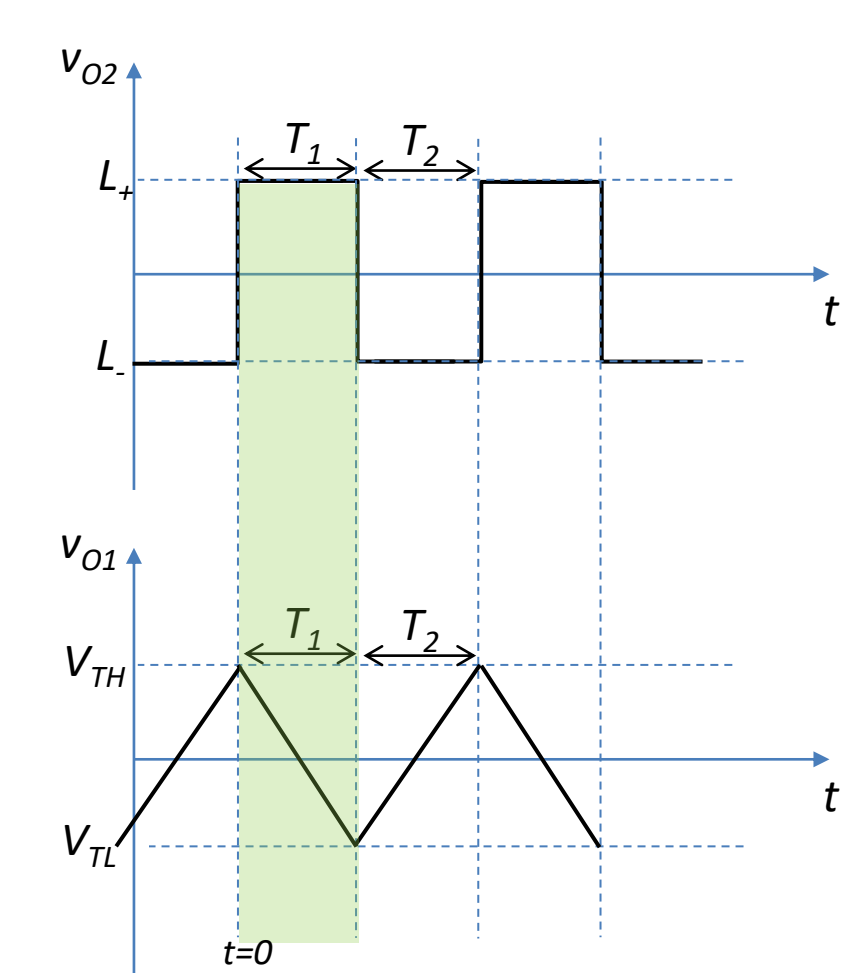

$$i = C \frac{dV_C}{dt} = -C \frac{dV_{O1}}{dt} = \frac{L_+}{R} \rightarrow \frac{dV_{O1}}{dt} = -\frac{L_+}{RC}$$
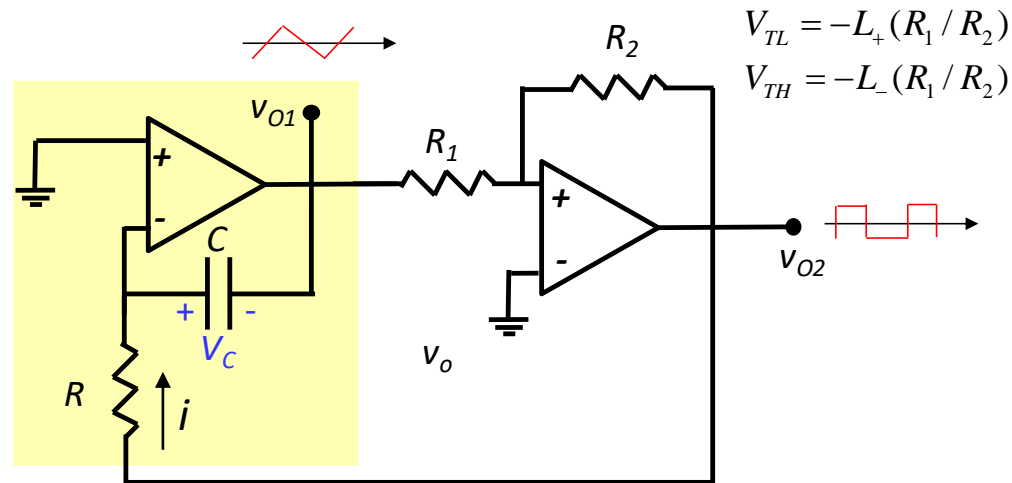
$$V_{O1}(t) = V_{TH} - \int \frac{L_+}{RC} dt = V_{TH} - \frac{L_+ t}{RC}$$



We can derive an expression for the period T of the square/triangular wave



During T_1 we have

$$\frac{V_{TH} - V_{TL}}{T_1} = \frac{L_+}{RC}$$

From which we obtain

$$T_1 = RC \frac{V_{TH} - V_{TL}}{L_+}$$

Generation of triangular waveforms

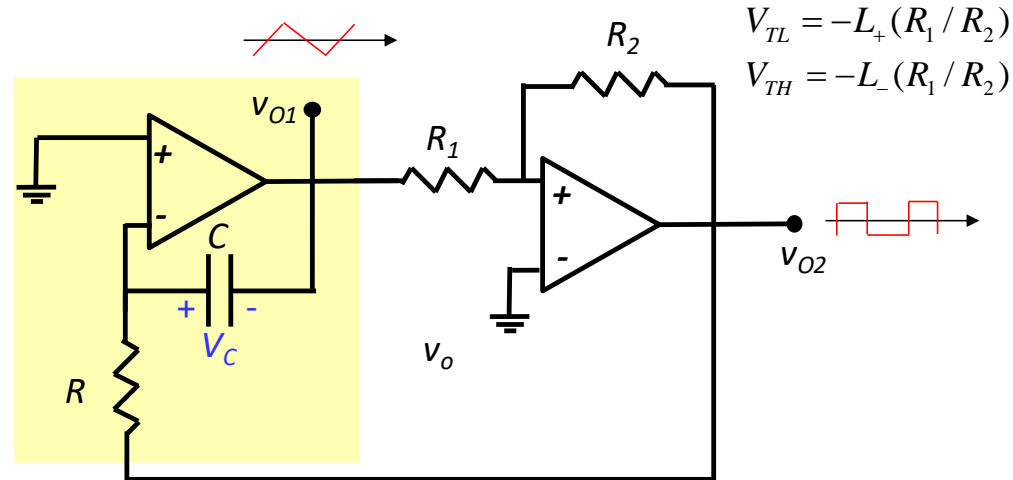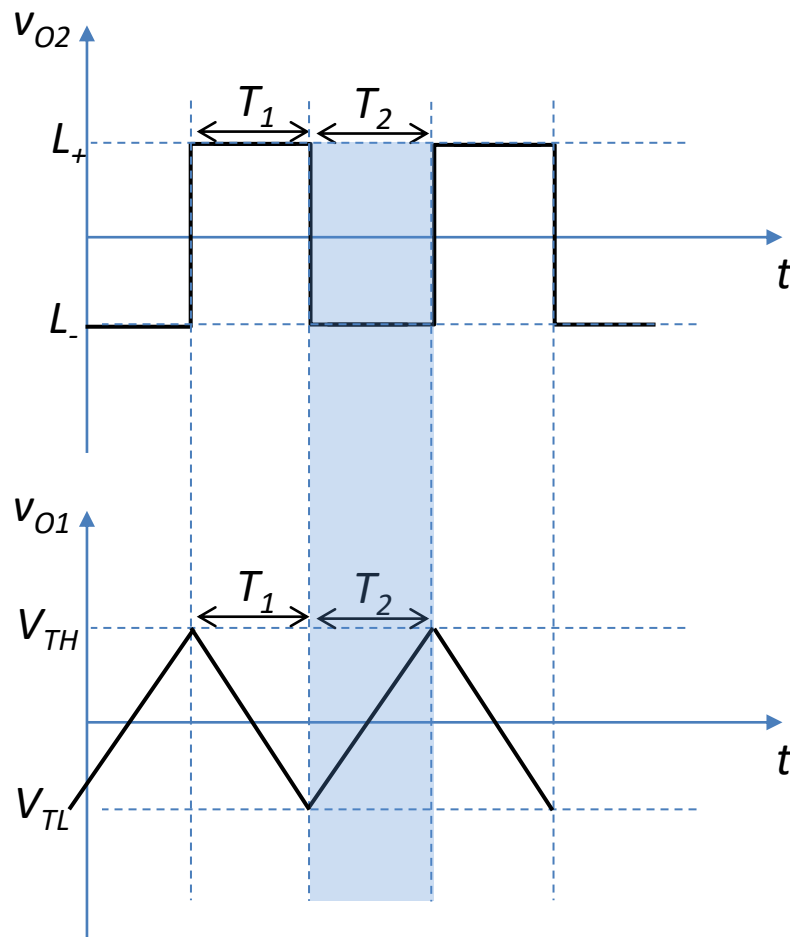

Similarly, during T_2 we have

$$\frac{V_{TH} - V_{TL}}{T_2} = \frac{-L_-}{RC}$$


From which we obtain

$$T_2 = RC \frac{V_{TH} - V_{TL}}{-L_-}$$

To obtain symmetrical waves we design the bistable circuit to have $L_+ = -L_-$

$$\longrightarrow T = T_1 + T_2 = 2RC \frac{V_{TH} - V_{TL}}{L_+}$$

Numerical example

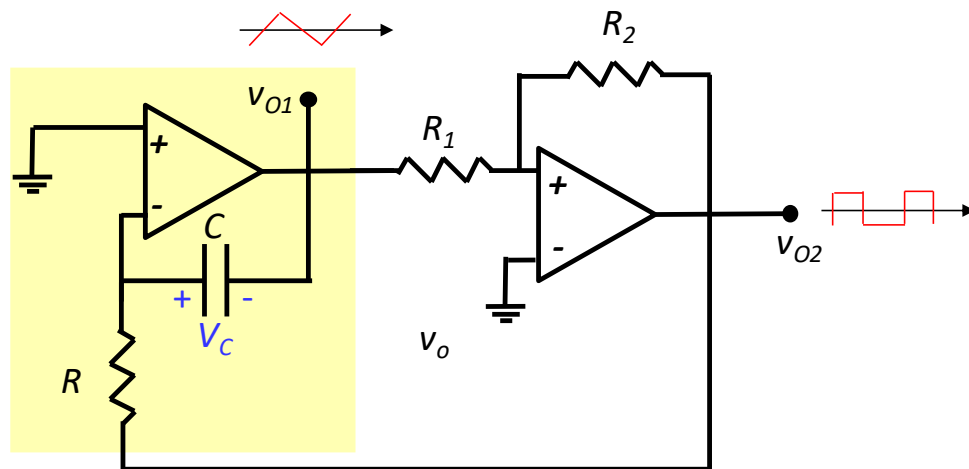

Considering the circuit in figure, the op-amps have saturation voltages of ± 10 V, a capacitor $C = 10$ nF and a resistor $R_1 = 10$ k Ω are used.

Find the values of R and R_2 such that the frequency of oscillation is 1 kHz and the triangular waveform has a 10 Vpp amplitude


Solution

We know that $T = \frac{1}{f} = 2RC \frac{V_{TH} - V_{TL}}{L_+} = 10^{-3} \text{ s} \rightarrow \text{Thus } R = \frac{L_+}{2fC(V_{TH} - V_{TL})} = 50 \text{ k}\Omega$


The non-inverting bistable circuit has $V_{TH} = |L_+ (R_1 / R_2)| = 5 \text{ V}$

We can therefore calculate
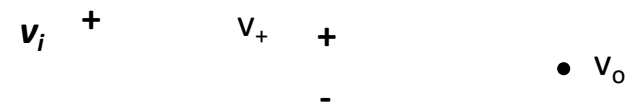
$$R_2 = \frac{L_+ R_1}{V_{TH}} = 20 \text{ k}\Omega$$



How to generate a sine wave?

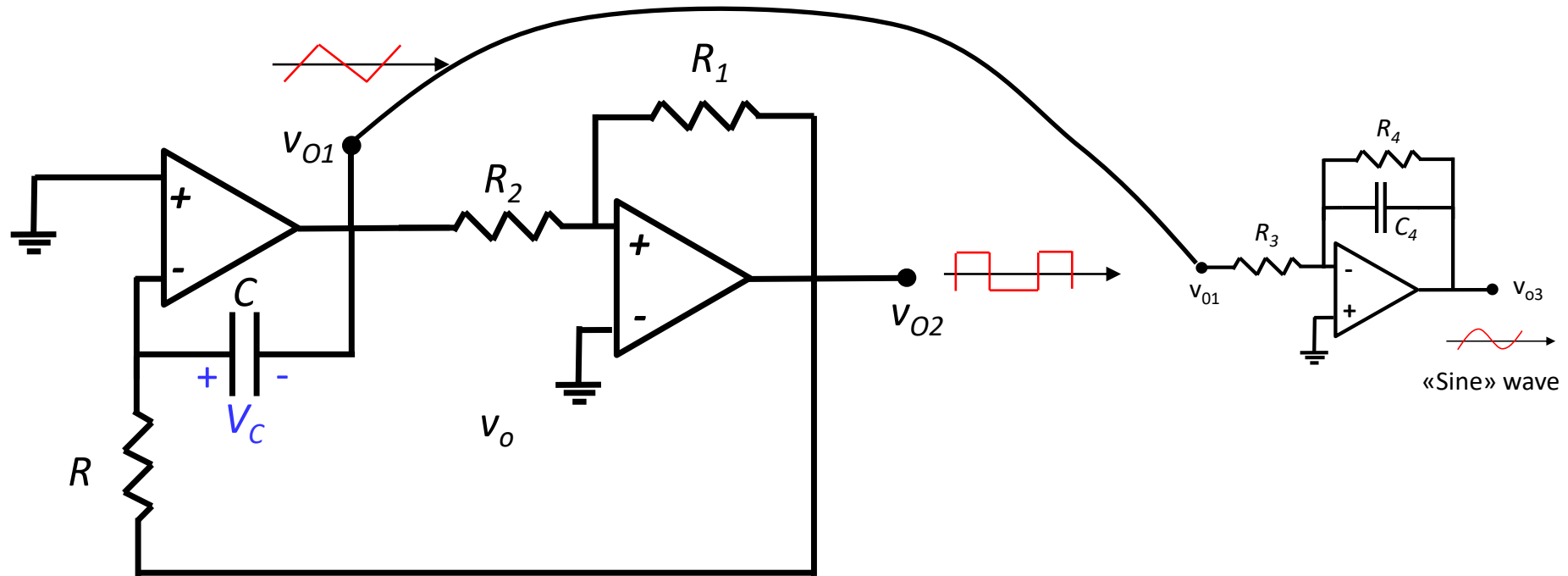


An effective way to create a sine wave is to start from a triangular wave and use a low-pass filter

This approach is relatively straightforward; the resulting sine-wave is not “ideal”, we will evaluate it in detail




Function generator based on the astable multivibrator

Low-pass filter (first order)

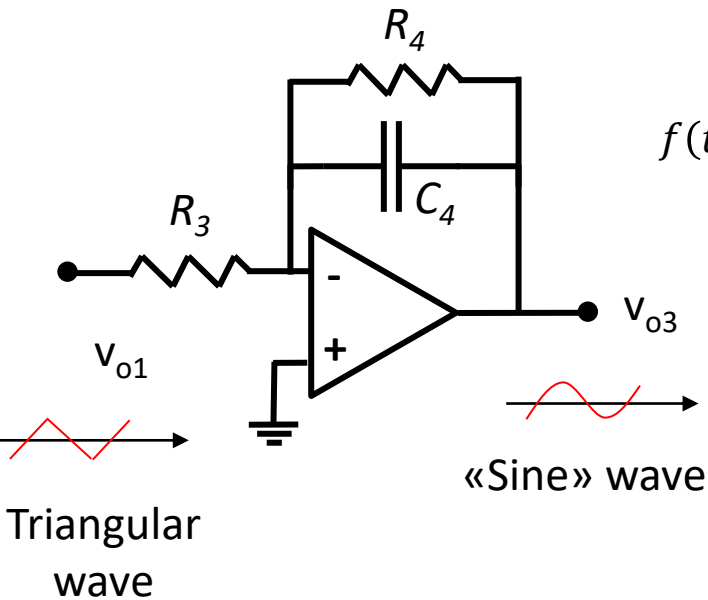

A triangular wave can be expressed as:

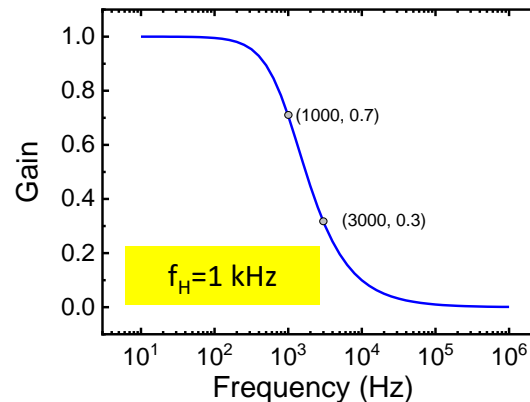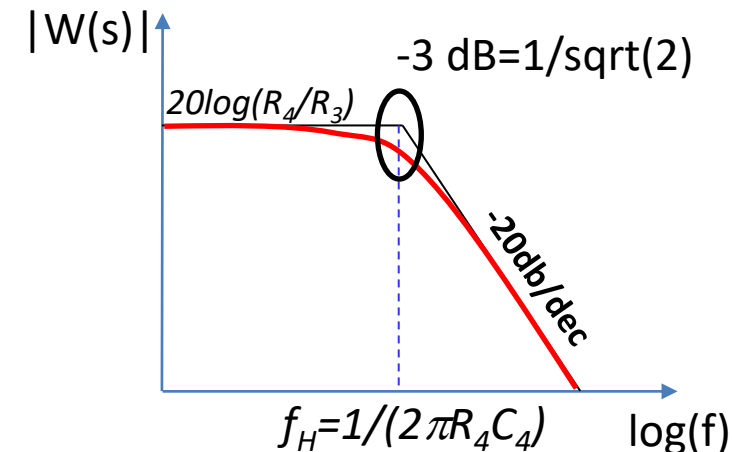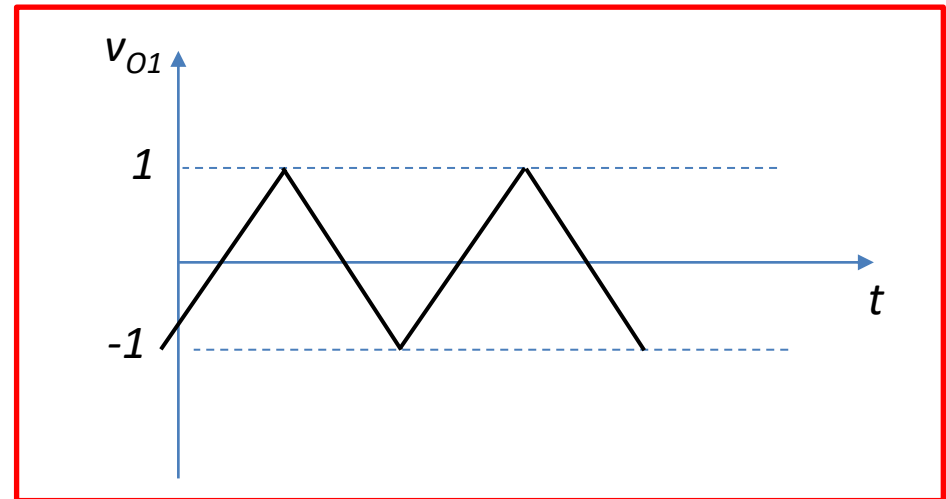
$$f(t) = \frac{8}{\pi^2} \left[\sin(\omega t) - \frac{1}{3^2} \sin(3\omega t) + \frac{1}{5^2} \sin(5\omega t) - \frac{1}{7^2} \sin(7\omega t) + \dots \right]$$



A simple low-pass filter may not be enough to obtain a good sine wave (3rd harmonic is attenuated to 30%)

From triangular wave to sine wave

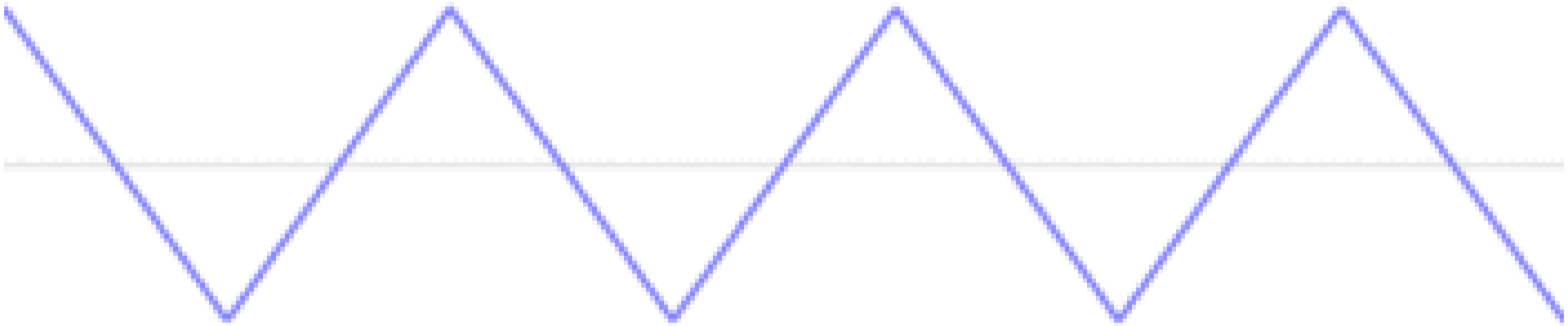
$$f(t) = \frac{8}{\pi^2} \left[\sin(\omega t) - \frac{1}{3^2} \sin(3\omega t) + \frac{1}{5^2} \sin(5\omega t) - \frac{1}{7^2} \sin(7\omega t) + \dots \right]$$



N = 0


https://en.wikipedia.org/wiki/File:Synthesis_triangle.gif

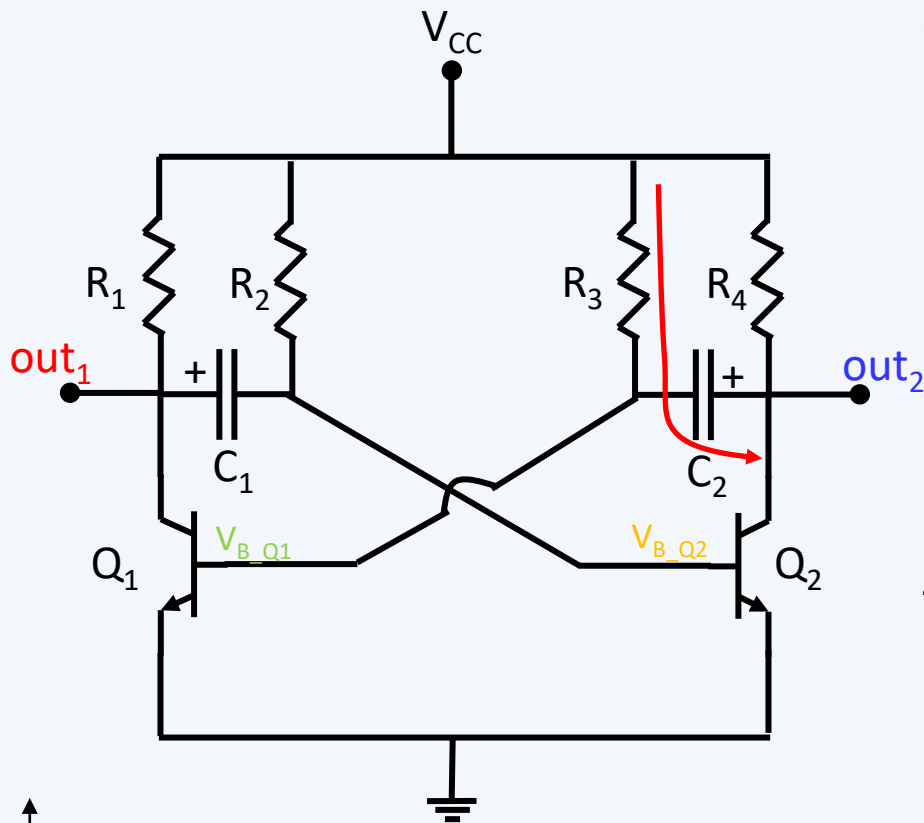Astable multivibrator without op-amps? (OPTIONAL)




Operating principle (simplified description)

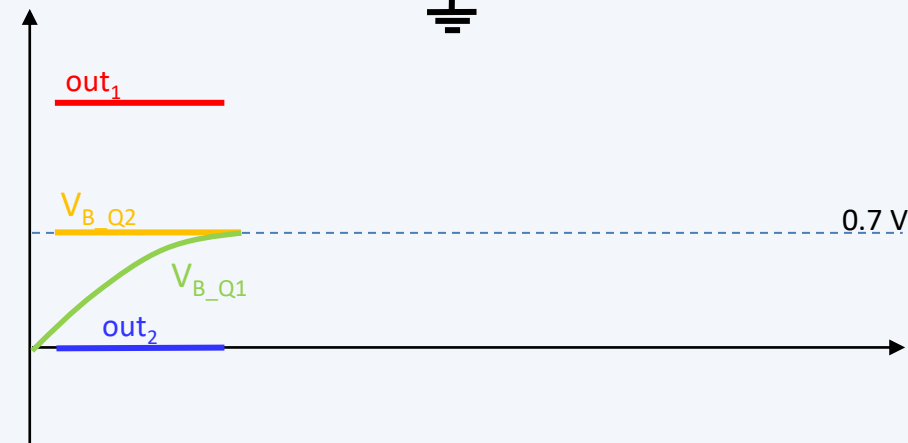1. Before power is applied, both BJTs are off
2. When power is applied, Q_1 and Q_2 should turn-on; one will be faster, due to small differences \rightarrow Assume it is $Q_2 \rightarrow V_{B_Q2}=0.7\text{ V}$
3. out_2 is then shorted to ground
4. Since C_2 is not charged yet, V_{B_Q1} is (initially) at ground potential, and Q_1 is off $\rightarrow out_1=V_{CC}$
5. C_2 starts charging through R_3 (time constant $=R_3C_2$), and V_{B_Q1} increases gradually until it reaches 0.7 V
6. At the same time, C_1 also charges, through R_1 , which is typically a small resistor (e.g. 100-1000 ohm). So C_1 's left lead (out_1) will quickly rise up to V_{CC} and remain high




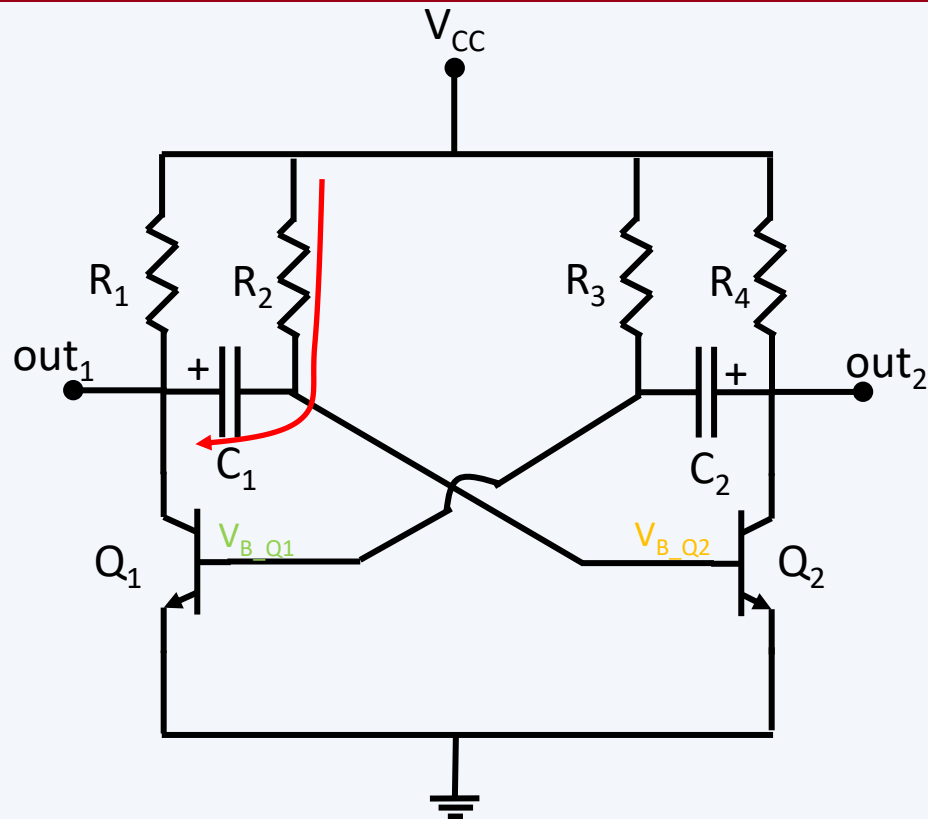Astable multivibrator without op-amps? (OPTIONAL)



Operating principle (simplified description)


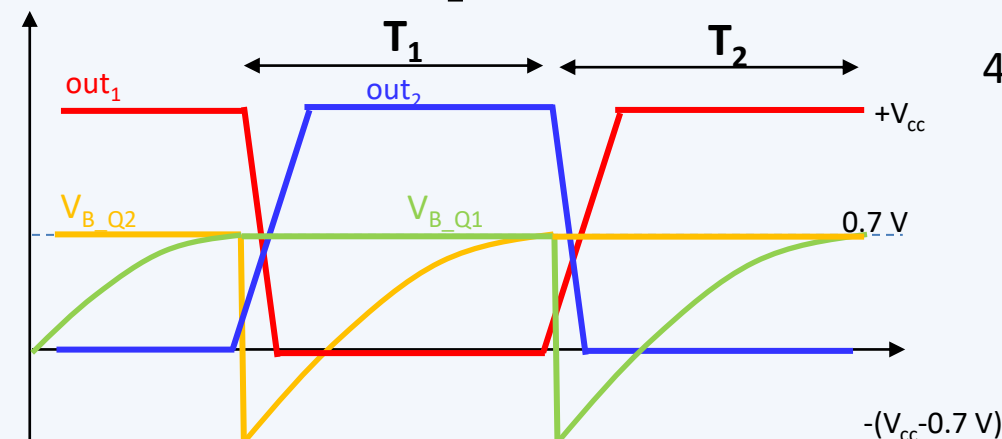
1. When V_{B_Q1} increases and reaches 0.7 V, Q_1 will turn on and its collector (out_1) will go to ground
2. Since C_1 's left lead is connected to Q_1 's collector, it will also drop to ground voltage
3. As C_1 is fully charged, its right lead (V_{B_Q2}) will suddenly drop to a negative voltage ($0.7\text{ V} - V_{CC}$). This will shut off Q_2 firmly
4. During this period, out_1 will remain low, and out_2 will quickly rise to V_{CC} (due to the charging of C_2 through a small resistor R_4)



It can be demonstrated that

$$t = T_1 + T_2 \sim \ln(2)(R_3 C_2 + R_2 C_1)$$

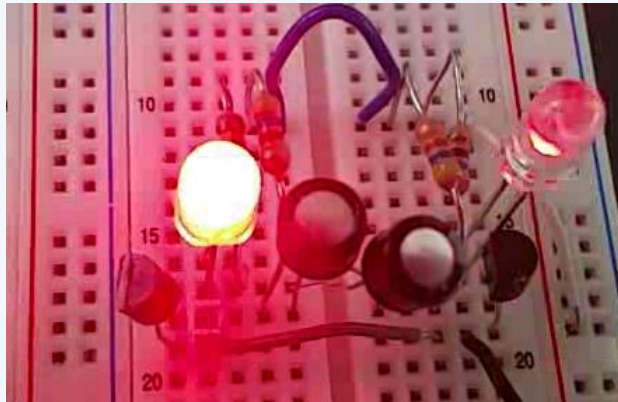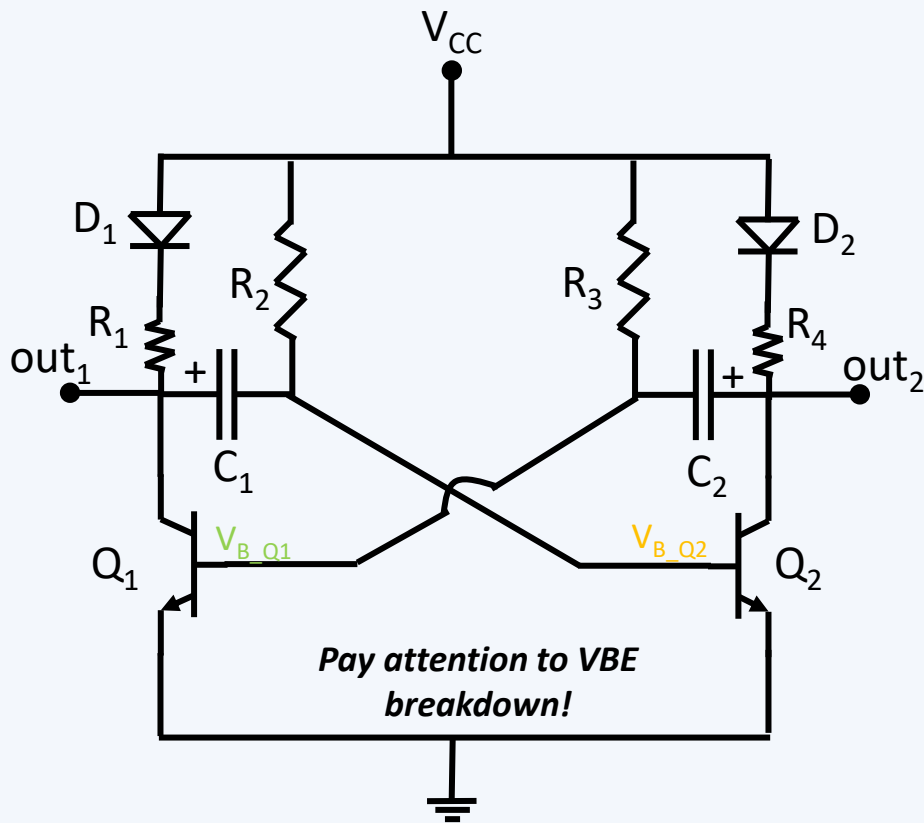Astable multivibrator without op-amps? (OPTIONAL)



This circuit blinks the two LEDs (D1 and D2) on and off continuously

1. Try this circuit with

$$R_1=R_4=470\ \Omega$$


$$R_2=R_3=47\ \text{k}\Omega$$

$$C_1=C_2=10\ \mu\text{F}$$

$$Q_1=Q_2=\text{BC548}$$

$$V_{CC}=9\ \text{V}$$

$$D_1=D_2=\text{red LEDs}$$

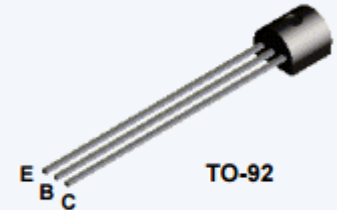

And measure the collector and base voltages of the two transistors as a function of time

2. How can the switching frequency be calculated? Explain in the report!

It can be demonstrated that if we add the LEDs

$$T = -\ln\left(\frac{V_{CC} - V_{BE}}{2V_{CC} - V_{BE} - V_{LED}}\right)(R_3C_2 + R_2C_1)$$

Source of these slides

The following texts have also been used to prepare this lecture:

- A. S. Sedra, and K. C. Smith, Microelectronic Circuits. Oxford, 2011
- R.C. Jaeger, T.N. Blalock, Microelettronica. McGraw-Hill
- Thomas L. Floyd, Electronic Devices. --: Pearson Prentice Hall, 2005
- P. Horowitz and W. Hill, The art of electronics. --: Cambridge University Press, 2015
- Neil Storey, Electronics, A system approach. --: Pearson Prentice Hall, 2006
- V. K. Mehta, Principles of Electronics